

CSE306  
4-bit ALU Simulation

Jawad Ul Kabir	Md. Mahfuzur Rahman Rifat
1705062	1705063

Taseen Mubassira	Ataf Fazledin Ahamed
1705065	1705066

Nishat Farhana Purbasha  
1705067

31 March, 2021

## 1 Introduction

An arithmetic logic unit (abbr. ALU) is a multi-operation, combinational-logic digital function- capable of performing a set of basic arithmetic operations and a set of logical operations. The ALU has a set of selection lines which enables a user to select a particular operation in the unit. The selection lines are decoded within the ALU so that  $k$  selection variables can specify up to  $2^k$  distinct operations.

## 2 Problem Specification with Assigned Instructions

Design a 4-bit ALU with three selection bits cs0, cs1 and cs2 for performing the following operations:

cs2	cs1	cin cs0	Functions
0	0	0	Decrement A
0	0	1	Transfer A
0	1	$\times$	OR
1	0	0	Subtract with Borrow
1	0	1	Subtract
1	1	$\times$	Complement A

## 3 Truth Table and K-maps

Truth table for the functions:

cs2	cs1	cs0	Function	$X_i$	$Y_i$	$Z_i$
0	0	0	$A - 1$	$A_i$	1	$C_i$
0	0	1	$A$	$A_i$	1	$C_i$
0	1	0	$A \text{ OR } B$	$A_i \vee B_i$	0	0
0	1	1	$A \text{ OR } B$	$A_i \vee B_i$	0	0
1	0	0	$A - B - 1$	$A_i$	$B'_i$	$C_i$
1	0	1	$A - B$	$A_i$	$B'_i$	$C_i$
1	1	0	$A'$	$A_i$	1	0
1	1	1	$A'$	$A_i$	1	0

**K-Map for  $X_i$ :**

		$s_1 s_0$				$s_1 s_0$			
		00	01	11	10	00	01	11	10
$A s_2$	00	0	0	0	0	0	0	1	1
	01	0	0	0	0	0	0	0	0
	11	1	1	1	1	1	1	1	1
	10	1	1	1	1	1	1	1	1
$B=0$						$B=1$			

$$X_i = A_i + B_i s'_2 s_1$$

**K-Map for  $Y_i$ :**

		$s_1 s_0$			
		00	01	11	10
$B s_2$	00	1	1	0	0
	01	1	1	1	1
	11	0	0	1	1
	10	1	1	0	0

$$Y_i = B'_i s_2 + s_2 s_1 + s'_2 s'_1$$

**K-Map for  $Z_i$ :**

		$s_2 s_1$			
		00	01	11	10
$C_i s_0$	00	0	0	0	0
	01	0	0	0	0
	11	1	0	0	1
	10	1	0	0	1

$$Z_i = C_i s'_1$$

## 4 Block Diagram

 


Figure 1: Block diagram of a 4 bit ALU

## 5 Complete Circuit Diagram

 


Figure 2: 1 Bit ALU

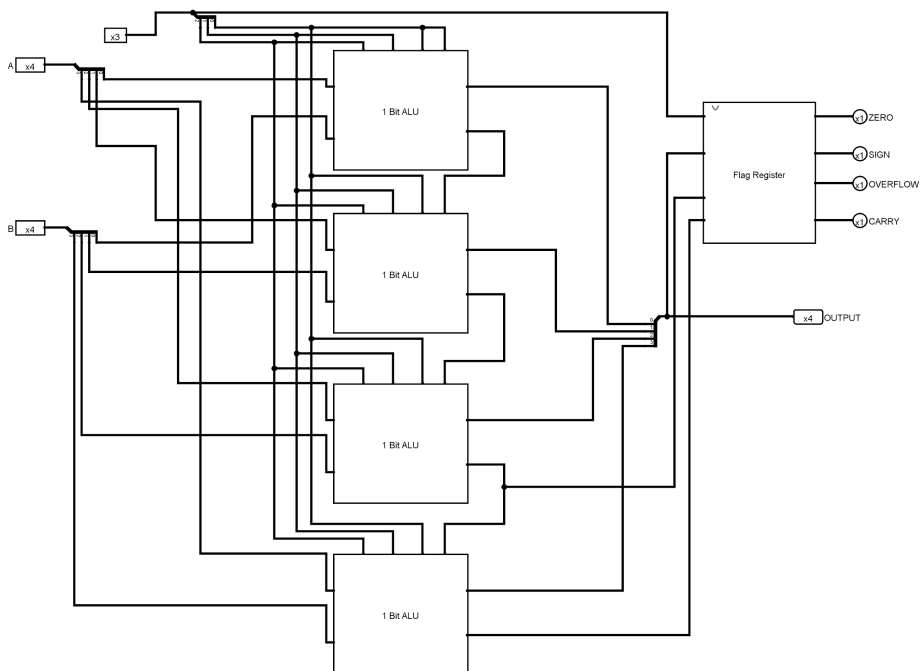


Figure 3: 4 Bit ALU

 


Figure 4: Flag Register

#### Additional combinational circuit for the Flag Register:

The Flag register requires the Carry flag (C) and the Overflow flag (V) to be cleared (0) after a logical OR operation. The ALU performs an OR operation when  $s_2=0$  and  $s_1=1$ ; Therefore,

The modified carry =  $C(s_2's_1)'$

The modified overflow =  $V(s_2's_1)'$

## 6 Total Number of ICs Used in the Implementation

Name	IC no.	Number of Gates	Number of ICs
OR	IC 7432	15	4
AND	IC 7408	27	7
NOT	IC 7404	15	4
Adder	IC 7483	4	4

## 7 Simulator Info

Logisim - Java Platform (Version 2.7.1)

## 8 Discussion

- We designed the ALU in Logisim simulator.
- Initially we designed an 1 bit ALU and from it by cascading we designed the 4 bit ALU according to the functions that were given as our task. And lastly, we designed a Flag register to show the values of C, S, Z and V flags. We combined the two circuits together and got the 4 bit ALU.
- For the designing of ALU according to the given functions, we formed a truth table, used it to construct the required k-maps for  $X_i$ ,  $Y_i$  and  $Z_i$ , derived equations for each of them and used the equations to design the 1 bit ALU.
- We used cs0 as our initial  $C_{in}$  bit and the other cs1 and cs2 as selector bits for the required arithmetic and logical operations.
- One important thing to mention here is that the flag register in the ALU does not fully comply with the rules of assembly language in the sense that the values of C, V, S or Z bits may change after a logical NOT operation even though assembly language rules clearly dictate that NOT operations should not affect the Flag register at all.